



2/17/2022

# Lab #3

Up down counter implemented on  
CL3641AH

Troy Scevers

CST 231 – DIGITAL SYSTEM DESIGN I

Troy Scevers

## Table of Contents

Abstract.....	2
Introduction .....	3
Design.....	3
Physical hardware design.....	3
Synthesized hardware design .....	4
Design Structure.....	4
Modules .....	5
Simulation and Testing.....	5
Problems .....	5
Results and Conclusion .....	5
Appendix .....	6
Table of Figures.....	11
References .....	12

## Abstract

The objective of this lab is to implement an up down counter on a muxed seven segment display component, the CL3641AH. The development board used is the Cyclone V. We are interfacing with the CL3641AH seven segment display. To do this, the GPIO\_0 on the development board will be used to interface with the component. I had serious problems completing this lab. The first issue was that my component was faulty. The B segment was bad, and the ones digit does not work. The second issue was my wiring. I initially wired the component wrong, leading to garbage being displayed. Overall, I found this lab to be very difficult. It was nice completing it, and it feels like I have learned a lot about different aspects of embedded design. One aspect that will help me in the future is troubleshooting. I have learned to not rely on just my code being faulty, but to also look at components and wiring. This lab helped me realize that timing is very important and metastability is bad. Although I had setbacks, I have learned a lot.

# Introduction

The objective of this lab is to implement an up down counter on a muxed seven segment display component, the CL3641AH. This lab allowed the student to learn about interfacing with third party components.

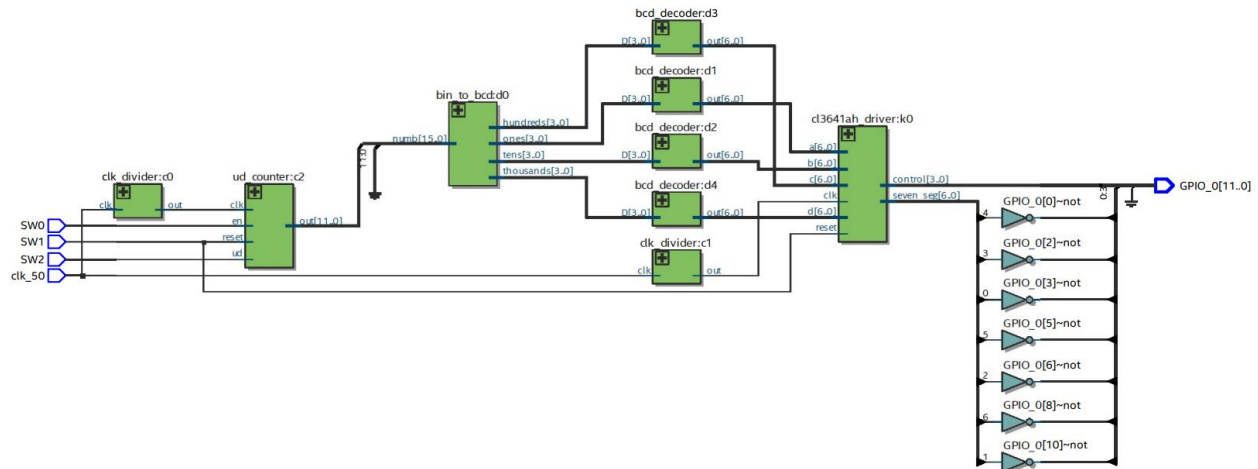


Figure 1: Top level block diagram of project

## Design

### Physical hardware design

The development board used is the Cyclone V. We are interfacing with the CL3641AH seven segment display. To do this, the GPIO\_0 on the development board will be used to interface with the component. See figure 2 for Cyclone pinout. The first twelve pins are used on GPIO\_0. Pins 11 and 12 must be skipped since they are ground and Vcc. The seven-segment display will be connected to each pin with a resistor, limiting the voltage. At 10 mA, the ideal voltage would be 1.8 V as shown in the component documentation.

Forward Voltage	VF	1.8		V	IF=10mA
-----------------	----	-----	--	---	---------

Figure 2: Forward Voltage of CL341AH

$$V_f = 1.8 V \text{ at } 10mA$$

$$v_{GPIO} = 3.3 V$$

$$i_{GPIO_{MAX}} = 1.5A$$

$$R = \frac{3.3 v - 1.8 v}{.010 A} = 150 \text{ ohm}$$

at 5mA

$$R = \frac{3.3 v - 1.8 v}{.005 A} = 300 \text{ ohms}$$

$$150 \leq R \leq 300$$

Figure 3: resistance calculations

It was found that the resistor should be between 150 and 300 ohms for proper voltage levels. To connect the component, a single resistor is placed between the CL3641AH and the GPIO\_0 pins. See figure below.



Figure 4: Wiring schematic

CL3641AH uses active high seven segment displays, but active low mux controls to display which digit. See figure 6 for the schematic for the seven-segment display. The top pins are used as controls for the internal mux. The bottom pins are the seven segment controls. This display uses a common cathode for the seven segments.

## Synthesized hardware design

### Design Structure

See figure 1 for top level block diagram. Three switches are used for enable, reset, and up down set. The board's clock is used to drive the logic. Two clock dividers are used to slow the clock. One regulates the counter and the other regulates the component's displays. An up down counter is used to count up or down. This output is sent to a binary to bcd decoder. This splits the number into ones, tens, hundreds, and thousands digits. These digits are sent to a bcd decoder. These outputs from the four bcd decoders feed into the CL3641AH driver. This driver handles the output to the component.

## Modules

### *Clk\_divider*

This module slows the clock to a given frequency. The input is the system clock. The output is the desired clock speed. See Lab 2 for more information about the clock divider.

### *Ud\_counter*

This module counts up or down. It counts up or down with a parameterized bit length. The inputs are clock, enable, reset, and updown. When updown is high, the module counts up. See figure 7 for ud\_counter RTL. See figure 8 for ud\_counter simulation.

### *Bin\_to\_bcd*

Converts 16-bit binary number to single digit bcd. See figure 9 for bin\_to\_bcd RTL. See figure 10 for bin\_to\_bcd simulation.

### *Bcd\_decoder*

Decodes single bcd digit to seven segment display encoding. See lab 2 for more details.

### *Cl3641ah\_driver*

Drives a muxed, 4 digit, seven segment display. The inputs for this module are a clock, a reset, and the data for each seven segment. The clock feeds into the mux controller that count. This count feeds into a controller for the mux in the component. It also feeds into a mux that chooses which digit to output. See figure 11 for RTL. See figure 12 for simulation.

## Simulation and Testing

See appendix for simulations of modules. All modules acted as specified in the section above.

## Problems

I had serious problems completing this lab. The first issue was that my component was faulty. The B segment was bad, and the ones digit does not work. The second issue was my wiring. I initially wired the component wrong, leading to garbage being displayed.

## Results and Conclusion

Overall, I found this lab to be very difficult. It was nice completing it, and it feels like I have learned a lot about different aspects of embedded design. One aspect that will help me in the future is troubleshooting. I have learned to not rely on just my code being faulty, but to also look at components and wiring. This lab helped me realize that timing is very important and metastability is bad. Although I had setbacks, I have learned a lot.

## Appendix

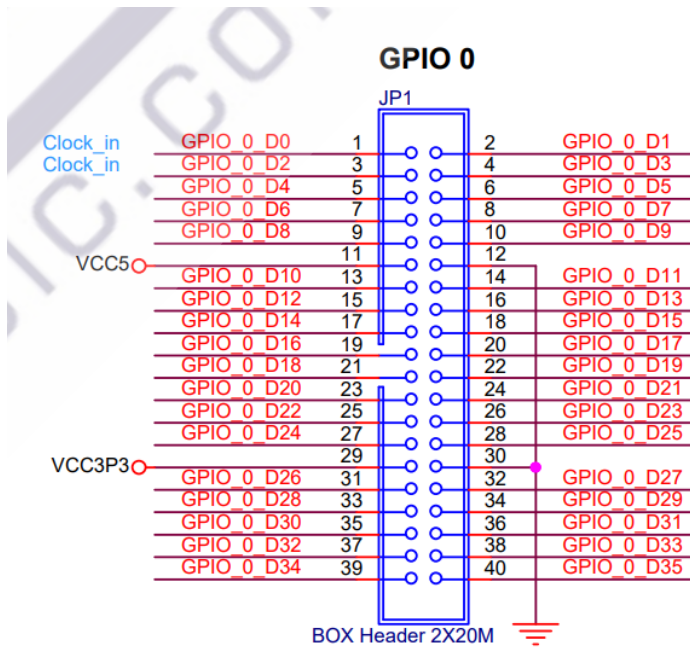


Figure 5: Cyclone V GPIO\_0 pinout

 


Figure 6: CL3641AH schematic

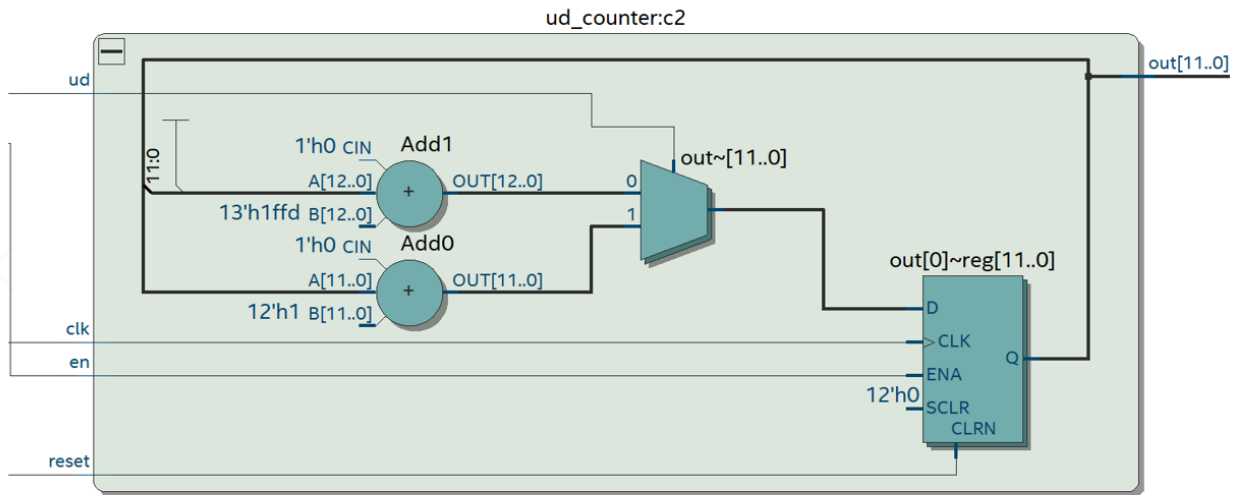


Figure 7: ud\_counter RTL

 


Figure 8: ud\_counter simulation

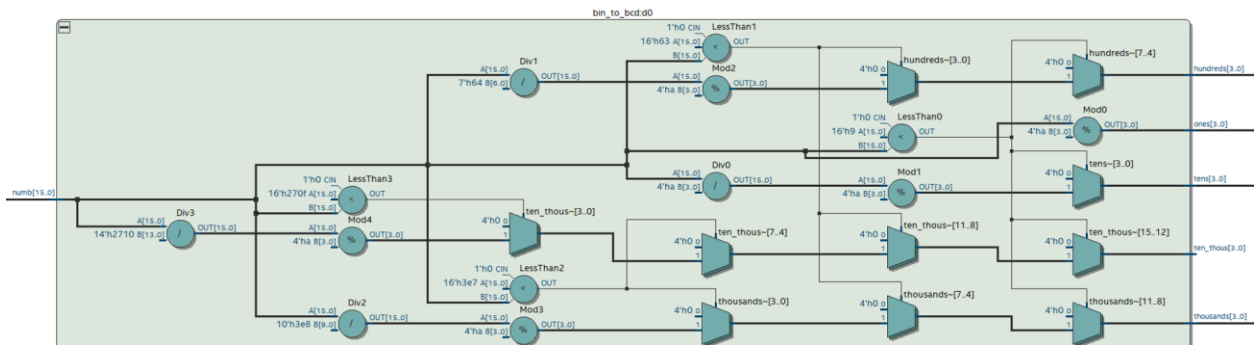


Figure 9: bin\_to\_bcd RTL

 


Figure 10: bin\_to\_bcd simulation



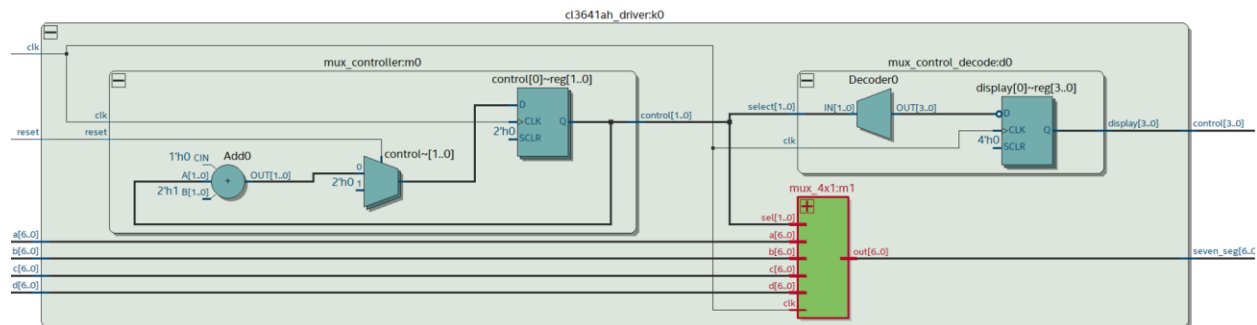


Figure 11: cl3641ah\_driver RTL

 


Figure 12: cl3641ah\_driver simulation



*Figure 13: pinout of lab 3*

## Table of Figures

Figure 1: Top level block diagram of project .....	3
Figure 2: Forward Voltage of CL341AH.....	3
Figure 3: resistance calculations .....	4
Figure 4: Wiring schematic .....	4
Figure 5: Cyclone V GPIO_0 pinout.....	6
Figure 6:CL3641AH schematic .....	6
Figure 7: ud_counter RTL.....	7
Figure 8: ud_counter simulation.....	7
Figure 9: bin_to_bcd RTL .....	7
Figure 10: bin_to_bcd simulation .....	7
Figure 11: cl3641ah_driver RTL.....	8
Figure 12: cl3641ah_driver simulation .....	8
Figure 13: pinout of lab 3.....	10

## References

“Reference designer,” *Verilog Example - Clock Divide by even number*. [Online]. Available: [http://www.referencedesigner.com/tutorials/verilogexamples/verilog\\_ex\\_04.php](http://www.referencedesigner.com/tutorials/verilogexamples/verilog_ex_04.php). [Accessed: 21-Jan-2022].

“CL3641AH documentation,” [online]. Available: <http://www.xlitx.com/datasheet/CL3641AH.pdf> [Accessed: 21-Jan-2022].